

## **MODULE 3 : BOOLEAN ALGEBRA AND LOGIC GATES**

Introduction, NAND and NOR operations, Exclusive –OR and Exclusive – NOR operations, Boolean Algebra Theorems and Properties , Standard SOP and POS form, Reduction of Boolean functions using Algebraic method, K - map method (2,3,4 Variable).Variable entered Maps, Quine Mc Cluskey, Mixed Logic Combinational Circuits and multiple output function Basic Digital Circuits: NOT,AND, OR,NAND,NOR,EX-OR,EX-NOR Gates.




## CHAPTER - 3

### Boolean Algebra & Logic Gates
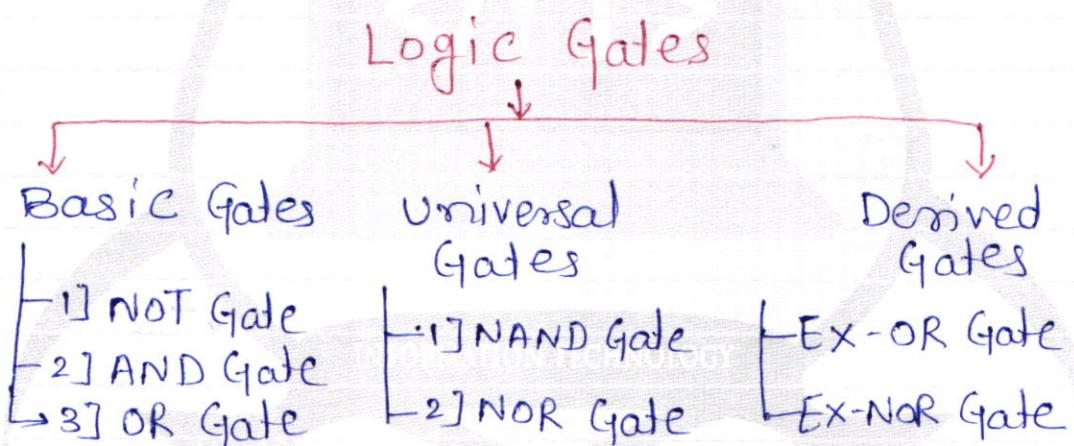
#### I] Logic Gates :-

- It is electronic ckt having one or more than one iIPs & only one oIP.
- It is logic ckt.
- It has classified into three categories



#### I] Basic Gates :-

##### I] NOT or Inverter [IC $\rightarrow$ 7404]

- This logic gate having one iIP & one oIP

symbol



Boolean eqn'

$$Y = \bar{A}$$

Truth Table

iIP	oIP
A	B
0	1
1	0



Semester: III


Subject: LD

Academic Year: 2017/18
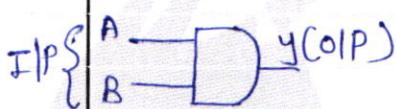
## 2] AND Gate $[IC \rightarrow 7408]$

- It performs logical multiplication on its I/O's

Symbol      Boolean Expression      Truth Table




$$y = A \cdot B$$

IIP	OIP
A	B
0	0
0	1
1	0
1	1
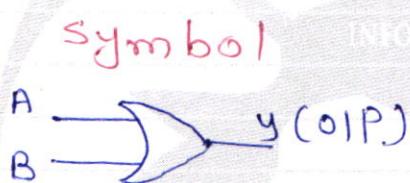
## 3) OR Gate

- It performs logical addition on its inputs.



Boolean Expression

$$y = A + B$$

Truth Table

IIP	OIP
A	B
0	0
0	1
1	0
1	1



Semester: III

Subject: LD

Academic Year: 17-18


## II] Universal Gates

- NAND & NOR gates are called universal gates because it is possible to implement any boolean expression with the help of NAND or only NOR gates.

### I] NAND Gate :- (NOT-AND)

- It is the combination of AND + NOT

Symbol

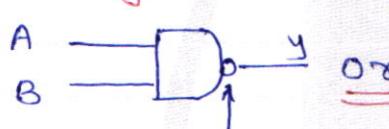

Bubble represents  
inversion

Boolean Expression

$$Y = \overline{A \cdot B}$$

Truth Table

	IP	OP
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

- Using NAND gate we can construct AND, OR & NOT gates.
- Truth Table - It shows OP is (0) low if & only if both IP's are high.
- It works complete opposite of AND gate



Semester: III

Subject: LD



Academic Year: 17-18

## II] NOR gate:

- It is the combination of an OR gate & NOT gate

$$\boxed{\text{OR} + \text{NOT} = \text{NOR}}$$

symbol

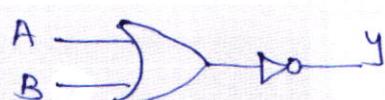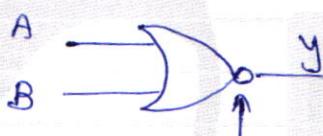

Bubble represents the inversion

Truth Table

Truth Table		
I/P	O/P	
A	B	y
0	0	1
0	1	0
1	0	0
1	1	0

- Boolean Expression

$$\boxed{y = \overline{A+B}}$$

- Truth Table :-

The O/P of a NOR gate is high (1) if and only if all its inputs are low (0).

- It works complete opposite of OR gate.



Semester: III

Subject: LD


Academic Year: 17-18

### III] Derived Gates (special type of gates)

#### 1] EX-OR gate - [Exclusive -OR gate) (X-OR)

- It can have two or more than two iIP's & one OIP terminal.


Symbol (2 iIP)

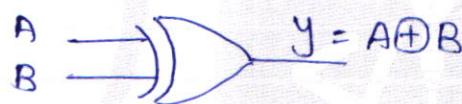

Truth Table

IIP		OIP
A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

symbol (4 iIP)

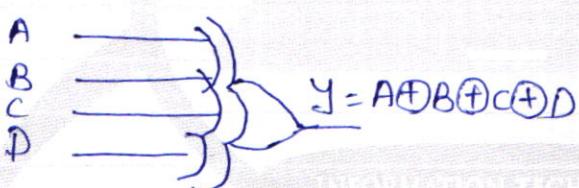

- If the iIP's are same then OIP will be 0 (zero.)

$$\text{i.e. } (A=B)=0$$

- If iIP's are different then OIP will be 1 (one)

$$A \neq B = 1$$



Semester: III


Subject: LD

Academic Year: 17-18

2] Ex-NOR Gate (Exclusive-NOR)  
(X-NOR)

- Ex-NOR gate is equivalent to an Ex-OR gate followed by a NOT gate

Symbol

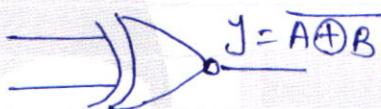

Truth Table

IIP		OIP
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

- If the IIP's are same then OIP will be 1 (one)

i.e. 
$$(A=B)=1$$

- If the IIP's are different then OIP will be 0 (zero)

i.e. 
$$A \neq B = 0$$



Semester: III

Subject: LD

Academic Year: 17-18

## \* Boolean Laws

### 1] Commutative law

$$1) A \cdot B = B \cdot A$$

$$2) A + B = B + A$$

### 2] Associative law

$$1) (A \cdot B) \cdot C = A \cdot (B \cdot C)$$

$$2) (A + B) + C = A + (B + C)$$

### 3] Distributive law

$$A \cdot (B + C) = AB + AC$$

### 4] AND Law

$$1) A \cdot 0 = 0$$

$$3) A \cdot A = A$$

$$2) A \cdot 1 = A$$

$$4) A \cdot \bar{A} = 0$$

3

### 5] OR Law

$$1) A + 0 = A$$

$$3) A + A = A$$

$$2) A + 1 = 1$$

$$4) A + \bar{A} = 1$$

### 6) Inversion Law

$$\overline{\overline{A}} = A$$



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

## 7) Other important law

- 1)  $A + BC = (A+B)(A+C)$
- 2)  $\bar{A} + AB = \bar{A} + B$
- 3)  $\bar{A} + A\bar{B} = \bar{A} + \bar{B}$
- 4)  $A + AB = A$
- 5)  $A + \bar{A}B = A + B$


### \* De-Morgan's Theorems :—

This theorems are extremely useful in Boolean algebra.
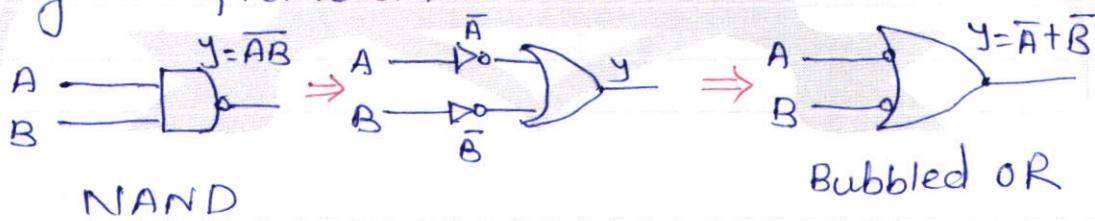
#### I] Theorem I -

$$\overline{AB} = \overline{A} + \overline{B} \quad (\text{NAND} = \text{Bubbled OR})$$

- It states that the complement of the product is equal to the addition of complements.



A	B	$\overline{AB}$	$\overline{A}$	$\overline{B}$	$\overline{A} + \overline{B}$
0	0	1	1	1	1
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	0

LHS  $\boxed{\overline{AB} = \overline{A} + \overline{B}}$



Semester: III


Subject: LD

Academic Year: 17-18
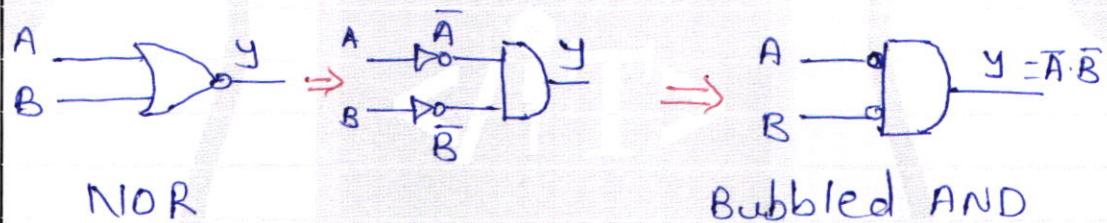
## II] Theorem II

$$\overline{A+B} = \overline{A} \cdot \overline{B} \quad (\text{NOR} = \text{bubbled AND})$$

- LHS represents a NOR gate with inputs A & B,
- RHS represents an AND gate with inverted inputs.



Truth Table

A	B	$\overline{A+B}$	$\overline{A}$	$\overline{B}$	$\overline{A} \cdot \overline{B}$
0	0	1	1	1	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	0

LHS  $\overline{A+B} = \overline{A} \cdot \overline{B}$  RHS



Semester: III

Subject: LD

Academic Year: 17-18

## \* Reducing the Boolean Expression

Prove the following expression

ex 1] To prove that  $(A+B)(A+C) = A+BC$

$$\rightarrow \text{LHS } (A+B)(A+C)$$

$$= AA + AC + BA + BC \rightarrow \text{Distributive Law}$$

But  $\rightarrow AA = A \rightarrow \text{AND law}$

$$= \underline{A+AC} + BA + BC$$

$$= A(1+c) + BA + BC \rightarrow 1+c = 1 \text{ OR Law}$$

$$= A + BA + BC$$

$$= A(1+B) + BC \rightarrow 1+B = 1 \text{ OR Law}$$

$$= A + BC$$

Thus 
$$(A+B)(A+C) = A+BC$$

ex2] Simplify  $ABCD + A\bar{B}CD$

$$\rightarrow Y = ABCD + A\bar{B}CD$$
$$= ACD(B + \bar{B}) \rightarrow B + \bar{B} = 1 \text{ OR Law}$$

$$Y = ACD$$



Semester: III

Subject: LD

Academic Year: 17-18

ex3]  $A\bar{B} + \bar{A}B + AB + \bar{A}\bar{B}$

Given  $y = \frac{A\bar{B}}{1} + \frac{\bar{A}B}{2} + \frac{AB}{1} + \frac{\bar{A}\bar{B}}{1}$

$$= \bar{B}(A + \bar{A}) + B(\bar{A} + A) \rightarrow A + \bar{A} = 1 \text{ OR Law}$$

$$= \bar{B} + B \rightarrow B + \bar{B} = 1 \text{ OR Law}$$

$$\therefore \boxed{y = 1}$$

4]  $A\bar{B}C + \bar{A}Bc + ABC$

Given  $y = \frac{A\bar{B}C}{1} + \frac{\bar{A}Bc}{1} + \frac{ABC}{1}$

$$= AC(\bar{B} + B) + \bar{A}BC \rightarrow \bar{B} + B = 1 \text{ OR Law}$$

$$= AC + \bar{A}BC$$

$$= C(A + \bar{A}B) \rightarrow A + \bar{A}B = A + B \text{ other law}$$

$$= C(A + B)$$

$$\boxed{y = C(A + B)}$$

5] Prove that  $AB + ABC + A\bar{B} = A$

LHS  $AB + ABC + A\bar{B}$   
=  $AB(1+C) + A\bar{B} \rightarrow (1+C) = 1 \text{ OR Law}$   
=  $AB + A\bar{B}$   
=  $A(B + \bar{B}) \rightarrow (B + \bar{B}) = 1$

$$= A$$

$$\therefore \boxed{AB + ABC + A\bar{B} = A}$$



Semester: III

Subject: LD

Academic Year: 17-18

6]  $xy + x(y+z) + y(y+z)$

→ given  $= xy + x(y+z) + y(y+z)$

Applying distributive law

$$A(B+C) = AB+AC$$

$$= xy + x\underline{y} + xz + \underline{y} \cdot y + yz$$

$$\rightarrow yy = y \text{ AND law}$$

$$= \underline{xy} + \underline{xy} + xz + y + yz$$

$$xy + xy = xy$$

$$= xy + xz + \underline{y} + yz \rightarrow$$

$$y + yz = y$$

$$= \underline{xy} + xz + \underline{y} \rightarrow$$

$$xy + y = y$$

$$\boxed{= y + xz}$$

7]  $xy + xyz + xy\bar{z} + \bar{x}yz$

→ Given

$$= xy + xyz + xy\bar{z} + \bar{x}yz$$

$$= xy(1+z) + xyz + \bar{x}yz \rightarrow (1+\bar{z}=1)$$

$$= \underline{xy} + \underline{xyz} + \underline{\bar{x}yz}$$

$$= xy + (1+\bar{z}) + \bar{x}yz \rightarrow 1+\bar{z}=1$$

$$= xy + \bar{x}yz \rightarrow x + \bar{x}z = x + z$$

$$= y(x+z)$$

$$\boxed{\therefore xy + yz}$$



Semester: III

Subject: LD

Academic Year: 17-18

8]  $ABC(\bar{C}\bar{D}) + (\bar{B}CD) + (\bar{A} + \bar{C})(B + D)$

$\Rightarrow$  Given  $\underline{ABC}\underline{(\bar{C}\bar{D})} + (\bar{B}CD) + (\bar{A} + \bar{C})(B + D)$

Using Demorgan's Theorem

$$= ABC(\bar{C} + \bar{D}) + (\bar{B}CD) + \bar{A}B + \bar{A}D + \bar{C}B + \bar{C}D$$

$$= AB\bar{C} + AB\bar{D} + \bar{B}CD + \bar{A}B + \bar{A}D + \bar{C}B + \bar{C}D$$

Rearrange the term

$$= \underline{AB\bar{C}} + \underline{B\bar{C}} + \underline{AB\bar{D}} + \underline{\bar{A}B} + \underline{\bar{B}CD} + \underline{\bar{C}D} + \underline{\bar{A}D}$$

$$= B\bar{C}(A+1) + B(\bar{A} + A\bar{D}) + D(\bar{B}C + \bar{C}) + \bar{A}D$$

$$\rightarrow A+1 = 1$$

$$\bar{A} + A\bar{D} = \bar{A} + \bar{D}$$

$$\bar{B}C + \bar{C} = \bar{B} + \bar{C}$$

$$= B\bar{C} + B(\bar{A} + \bar{D}) + D(\bar{B} + \bar{C} + \bar{A}D)$$

$$= \underline{B\bar{C}} + \underline{B\bar{A}} + \underline{B\bar{D}} + \underline{D\bar{B}} + \underline{D\bar{C}} + \underline{\bar{A}D}$$

$$= B(\bar{C} + \bar{A} + \bar{D}) + D(\bar{B} + \bar{C} + \bar{A})$$

Using Demorgan's Theorem

$$= B(\overline{ACD}) + D(\overline{ABC})$$

$$\boxed{B(\overline{ACD}) + D(\overline{ABC})}$$



Semester: III

Subject: LD

Academic Year: 17-18

g]  $A[B+C(\overline{AC}+\overline{AB})]$

→ Given  $A[B+C(\overline{AC}+\overline{AB})]$

Demorgan's Theorem

$$= A[B+C(\overline{A}+\overline{C})(\overline{A}+\overline{B})]$$

$$= A[B+C(\overline{A}\overline{A}+\overline{A}\overline{B}+\overline{C}\overline{A}+\overline{C}\overline{B})]$$

$\rightarrow \overline{A}\overline{A} = \overline{A}$

$$= A[B+C(\overline{A}+\overline{A}\overline{B}+\overline{C}\overline{A}+\overline{C}\overline{B})]$$

$$= A[B+C[\overline{A}(1+\overline{B})+\overline{C}\overline{A}+\overline{C}\overline{B}]]$$

$$= A[B+C(\overline{A}+\overline{C}\overline{A}+\overline{C}\overline{B})] \quad \because 1+\overline{B}=1$$

$$= A[B+C(\overline{A}+\overline{C}\overline{B})]$$

$$= A[B+C(\overline{A}(1+\overline{C})+\overline{C}\overline{B})]$$

$$= A[B+C(\overline{A}+\overline{C}\overline{B})] \quad \because 1+\overline{C}=1$$

$$= A[B+\overline{A}\overline{C}+\overline{B}\overline{C}\overline{C}]$$

$$= A[B+\overline{A}\overline{C}+\overline{B}\overline{C}] \quad \because \overline{C}\cdot\overline{C}=0$$

$$= A[B+\overline{A}\overline{C}]$$

$$= AB+A\overline{A}\overline{C} \quad \because A\cdot\overline{A}=0$$

$$\boxed{= AB}$$



Semester: III

Subject: LD

Academic Year: 17-18

10] Prove & draw the logic diagram

$$\bar{A}BC + A\bar{B}C + AB\bar{C} + ABC = AB + BC + AC$$

$$\rightarrow LHS = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

Rearranging the terms

$$= \underline{\bar{A}BC} + ABC + A\bar{B}C + AB\bar{C}$$

$$= BC(\bar{A} + A) + A\bar{B}C + AB\bar{C} \rightarrow [A + \bar{A} = 1]$$

$$= \underline{BC} + A\bar{B}C + AB\bar{C}$$

$$= C(\underline{B + A\bar{B}}) + AB\bar{C} \rightarrow [A + \bar{A}B = A + B]$$

$$= \underline{C(A+B)} + AB\bar{C}$$

$$= AC + BC + AB\bar{C}$$

Rearrange the terms


$$= \underline{AC + AB\bar{C} + BC}$$

$$= A(\underline{C + B\bar{C}}) + BC \rightarrow [A + \bar{A}B = A + B]$$

$$= A(\underline{B + C}) + BC$$

$$= AB + AC + BC$$

$$LHS = RHS$$

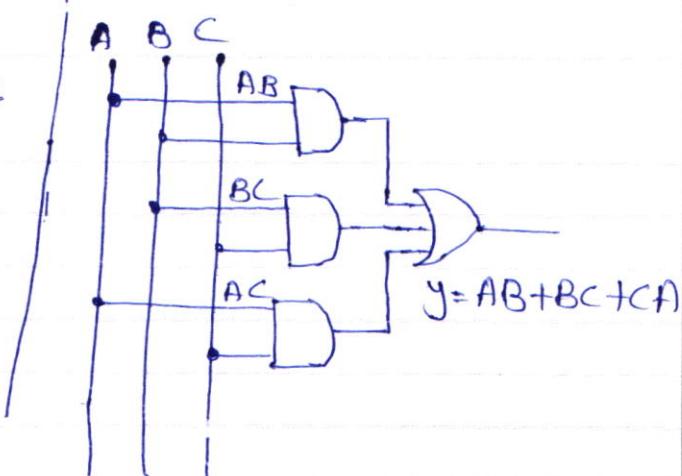



Semester: III

Subject: LD


Academic Year: 17-18

II] Draw the combinational circuit using the basic gates to obtain the following output.


$$Y = AB + BC + \bar{A}\bar{B}$$

→ This circuit has three inputs

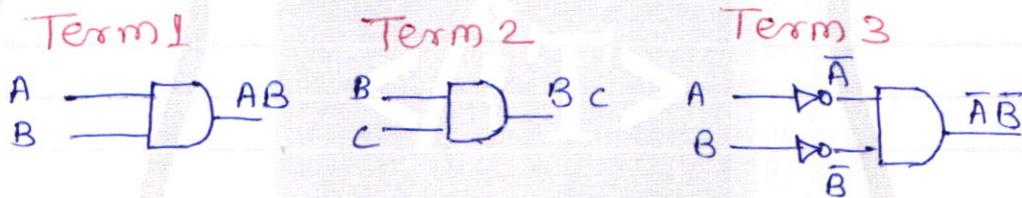Step I : Implement the three individual terms



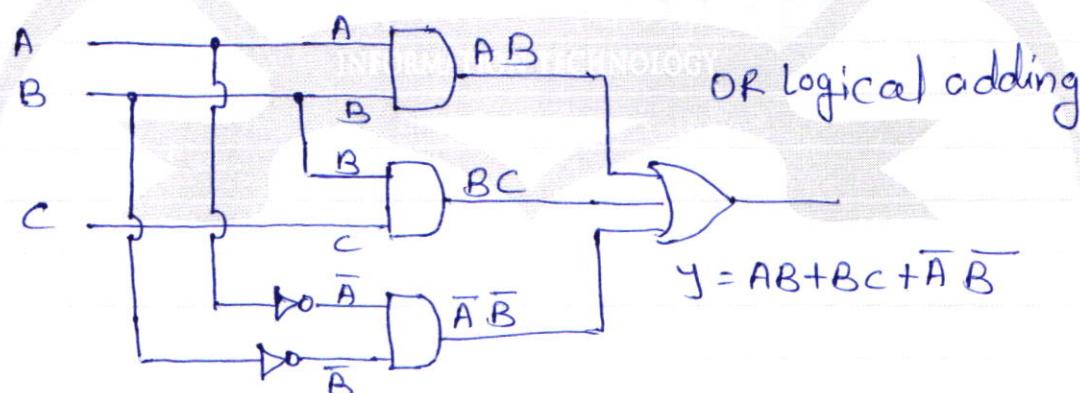Step II : Logically add the OIP of the three circuits





Semester: III

Subject: LD

Academic Year: 17-18

Q12] Simplify using Boolean theorems & draw logic diagram for the following

$$Y = \overline{AB}(B+C) + AB(\overline{B}+\overline{C})$$

$$\rightarrow Y = \overline{AB}(B+C) + ABC(\overline{B}+\overline{C})$$

by using DeMorgan's theorem


$$\begin{aligned} \overline{AB} &= \overline{A} + \overline{B} \\ \overline{B+C} &= \overline{B} \cdot \overline{C} \end{aligned}$$

$$= (\overline{A} + \overline{B})(B+C) + AB(\overline{B} \cdot \overline{C})$$

$$= \overline{AB} + \overline{AC} + \overline{B}B + \overline{BC} + AB\overline{B}\overline{C} \rightarrow [\overline{B} \cdot B = 0]$$

$$= \overline{AB} + \overline{AC} + \overline{BC}$$
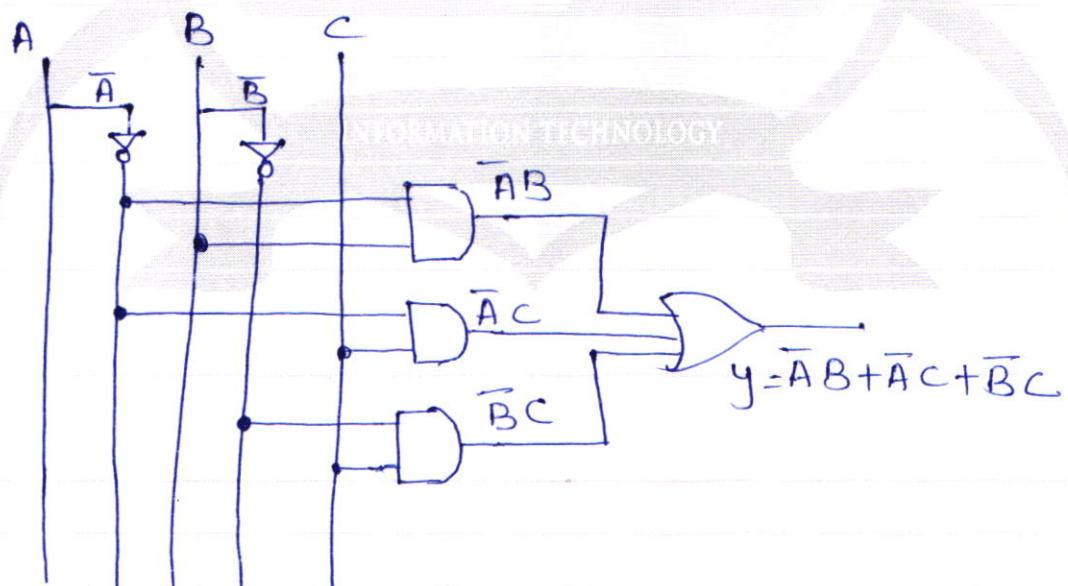
$$\boxed{\text{Ans} = \overline{AB} + \overline{AC} + \overline{BC}}$$





Semester: III


Subject: LD

Academic Year: 17-18

\* Standard presentation for logical function

- Logic Expression

$$y = AC + BC$$

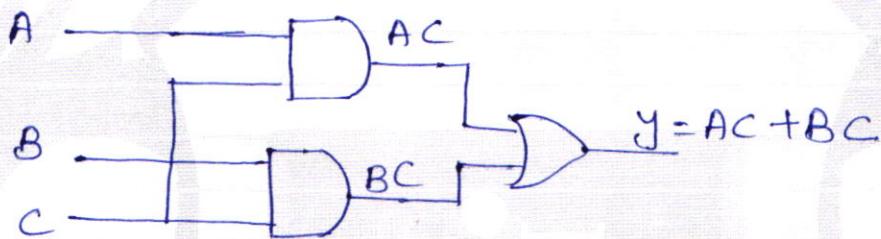

Here, Input variables are A, B & C  
& that variables are called literals.

IIP  $\rightarrow$  A, B, C  $\rightarrow$  Literals

1] Sum-of-Products (SOP) Form

2] Product-of-Sums (POS) Form



Semester: III

Subject: LD

Academic Year: 17-18

## I] sum-OF-products Form (SOP)

$$Y = AB + BC + AC$$

sum  
 product terms

- This type of expression are called as SOP
- Not actual additions or multiplications
- They are OR & AND functions
- A, B & C are called literals or input of combinational circuit.

Ex]

$$Y = xy + yz + zx$$

$$Y = PQR + QRS + RSP$$

$$A = \bar{x}y + y\bar{z} + z\bar{x}$$

## II] Product-Of-Sums (POS) Form

$$Y = (A+B) \cdot (B+C) \cdot (A+C)$$

products  
 sum terms

- These literals are ORed together to form the sum terms & the sum terms are ANDed to get the expression in the POS Form.



Semester: III

Subject: LD

Academic Year: 17-18

\* Standard or Canonical SOP & POS Form

- Each term contains all the iIP variables are called as standard or canonical

ex 1] Canonical SOP

$$y = \underbrace{ABC}_{\text{1}} + \underbrace{A\bar{B}C}_{\text{2}} + \underbrace{\bar{A}BC}_{\text{3}}$$

Each term contains all iIP variables  
& each individual term is called min term

ex 2] Canonical POS

$$Y = (A+B) \cdot (\bar{A}+B)$$

Each term contains all iIP variables  
& each individual term is called max term



Semester: III

Subject: LD

Academic Year: 17-18

### \* Non-standard Forms

- In this form each term may contain one, two or any number of literals.
- It means that, every literals does not appear in each term.
- It is not necessary that each term should contain all the literals.

#### 1] Non-standard SOP Form

$$y = AB + ABC\bar{C} + \bar{A}BC$$

#### 2] Non-standard POS Form

$$y = (\bar{A} + B) \cdot (A + B + C)$$



Semester: III

Subject: LD

Academic Year: 17-18

\* Conversion of Forms

I] Non-Standard SOP to Standard SOP Form

Steps

- 1] Find the missing literal for each term in the given non-standard SOP expression
- 2] Then AND this term with the term formed by ORing the missing literal & its compliment.
- 3] Simplify the expression to get the standard SOP expression.


Ex: Convert the expression

$y = AB + A\bar{C} + BC$  into the standard SOP Form

Given  $y = AB + A\bar{C} + BC$

In this eq<sup>n</sup> or expression has 3-IP variables A, B & C

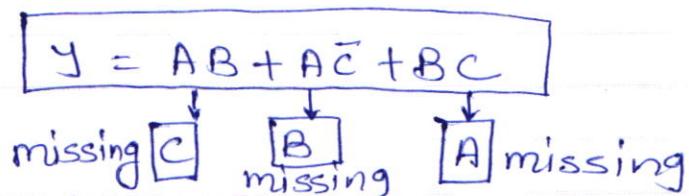Step I - Find the missing literal in each term





Semester: III

Subject: LD

Academic Year: 17-18

Step 2: AND each term with (missing literal + its complement)

$$y = AB \cdot (C + \bar{C}) + A\bar{C} \cdot (B + \bar{B}) + BC \cdot (A + \bar{A})$$

original  
product  
term

[missing literal + its complement]

Step 3: simplify the expression to get the std. pos form.

$$y = AB \cdot C(C + \bar{C}) + A\bar{C} \cdot (B + \bar{B}) + BC \cdot (A + \bar{A})$$

$$= \underbrace{ABC}_{1} + \underbrace{AB\bar{C}}_{2} + \underbrace{ABC}_{1} + \underbrace{A\bar{B}\bar{C}}_{1} + \underbrace{ABC}_{1} + \underbrace{\bar{A}\bar{B}C}_{1}$$

$$\therefore \underbrace{ABC}_{1} + \underbrace{ABC}_{1} = ABC$$
$$\underbrace{AB\bar{C}}_{1} + \underbrace{A\bar{B}\bar{C}}_{1} = A\bar{B}\bar{C}$$

$$y = ABC + AB\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{B}C$$

std  
SOP  
Form

Each term contains all the literals.

Ex2] convert in standard SOP form

$$A\bar{B}C + B\bar{D}$$

→ Given  $A\bar{B}C + B\bar{D}$



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

$$\begin{array}{c} A\bar{B}C + B\bar{D} \\ \downarrow \quad \downarrow \\ \boxed{D} \quad \boxed{A \& C} \\ \text{missing literals.} \end{array}$$

$$= A\bar{B}C(D+\bar{D}) + B\bar{D}(A+\bar{A})(C+\bar{C})$$

$$= A\bar{B}CD + A\bar{B}C\bar{D} + [A\bar{B}\bar{D} + \bar{A}B\bar{D} (C+\bar{C})]$$

$$\boxed{\begin{aligned} &= A\bar{B}CD + A\bar{B}C\bar{D} + A\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D} \\ &\quad + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}\bar{D} \end{aligned}}$$

Standard SOP Form

3]  $y = A+B$

Given  $y = A+B$

Missing literal

$$\begin{array}{c} A + B \\ \downarrow \quad \downarrow \\ \text{missing } \boxed{B} \quad \boxed{A} \text{ missing} \end{array}$$

$$= A(B+\bar{B}) + B(A+\bar{A})$$

$$= \underline{AB} + \underline{A\bar{B}} + \underline{A\bar{B}} + \underline{\bar{A}B}$$

$$\boxed{= AB + A\bar{B} + \bar{A}B} \rightarrow \text{Std sop form}$$

$$\therefore AB + AB = AB$$



Semester: III

Subject: LD

Academic Year: 17-18

II]

Conversion From Non-standard POS  
to standard POS Form

Steps

- 1] Find the missing literal for each term
- 2] OR each term with (Missing literal + its complement)
- 3] Simplify the expression to get std. pos

ex)]


Convert the expression

$y = (A+B)(A+C)(B+\bar{C})$  into std pos Form

→

Given  $y = (A+B)(A+C)(B+\bar{C})$

Step I

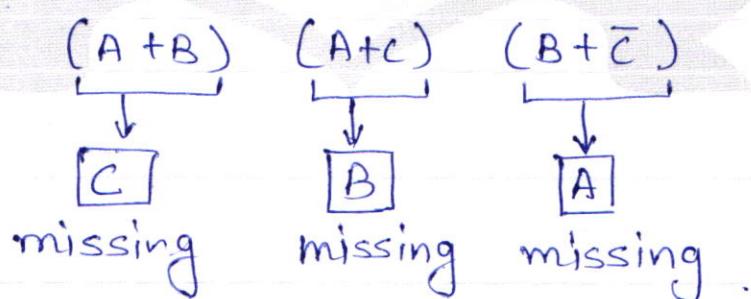

Step II :  $y = (A+B+C\bar{C})(A+C+B\cdot\bar{B})(B+\bar{C}+A\cdot\bar{A})$

↓  
missing literal term & its complement



Semester: III

Subject: LD

Academic Year: 17-18

Step III simplify the expression

$$y = (A+B+C\bar{C}) \cdot (A+C+B \cdot \bar{B}) (B+\bar{C}+A \cdot \bar{A})$$

$$\rightarrow A+B C = (A+B) (A+C)$$

$$= \underbrace{(A+B+C)}_1 \underbrace{(A+B+\bar{C})}_2 \underbrace{(A+B+C)}_1 (A+\bar{B}+C)$$

$$\underbrace{(A+B+\bar{C})}_2 (A+\bar{B}+\bar{C})$$

$$= \therefore (A+B+C)(A+B+C) = A+B+C$$
$$\therefore (A+B+\bar{C})(A+\bar{B}+\bar{C}) = A+B+\bar{C}$$

$$y = (A+B+C) (A+B+\bar{C}) (A+\bar{B}+C) (\bar{A}+B+\bar{C})$$

This is std POS Form. Each term contains all literals.

Ex2] Convert the given expression in std POS Form

$$f(ABC) = (A+B) (B+C) (A+C)$$

Given expression

$$F(ABC) = (A+B) (B+C) (A+C)$$

↓      ↓      ↓  
C      A      B  
missing   missing   missing



Semester: III

Subject: LD

Academic Year: 17-18

## \* Canonical Forms of Boolean Expressions

- 1] Minterm
- 2] Maxterm

### I) Minterm:

- It is used into the std sop Form.

ex) std sop

$$y = \underbrace{ABC}_{\text{minterm}} + \underbrace{A\bar{B}\bar{C}}_{\text{minterm}} + \underbrace{\bar{A}B\bar{C}}_{\text{minterm}}$$

Each individual term is called minterm

### II) Maxterm:

- It is used into the std pos Form

ex) std pos

$$\underbrace{(A+B)}_{\text{maxterm}} \underbrace{(B+A)}_{\text{maxterm}}$$

Each individual term is called Maxterm.



Semester: \_\_\_\_\_

Subject: LD

Academic Year: \_\_\_\_\_

Table For Minterm

IIP variables			Minterms (SOP)
A	B	C	
0	0	0	$\bar{A}\bar{B}\bar{C} = m_0$
0	0	1	$\bar{A}\bar{B}C = m_1$
0	1	0	$\bar{A}B\bar{C} = m_2$
0	1	1	$\bar{A}BC = m_3$
1	0	0	$A\bar{B}\bar{C} = m_4$
1	0	1	$A\bar{B}C = m_5$
1	1	0	$AB\bar{C} = m_6$
1	1	1	$ABC = m_7$

Table for Maxterm

IIP variables			Maxterm (POS)
A	B	C	
0	0	0	$A+B+C = M_1$
0	0	1	$A+B+\bar{C} = M_2$
0	1	0	$A+\bar{B}+C = M_3$
0	1	1	$A+\bar{B}+\bar{C} = M_4$
1	0	0	$\bar{A}+B+C = M_5$
1	0	1	$\bar{A}+B+\bar{C} = M_6$
1	1	0	$\bar{A}+\bar{B}+C = M_7$
1	1	1	$\bar{A}+\bar{B}+\bar{C} = M_8$

- Minterm always represents in small letter (m).
- Maxterm always represents in Capital letter (M).





Semester: \_\_\_\_\_

Subject: LD

Academic Year: \_\_\_\_\_

\* Representation of logical expressions using minterms & maxterms.

ex 1]  $y = ABC + \bar{A}BC + A\bar{B}\bar{C} \rightarrow (\text{SOP})$

Given:

$$\begin{array}{c} ABC + \bar{A}BC + A\bar{B}\bar{C} \\ \downarrow \quad \downarrow \quad \downarrow \\ m_7 \quad m_3 \quad m_4 \end{array}$$

Corresponding minterms

$$y = m_3 + m_4 + m_7$$

$$y = \sum m(3, 4, 7) \rightarrow \text{Summation of Minterm representation}$$

ex 2]  $y = (A + \bar{B} + C)(A + B + C)(\bar{A} + \bar{B} + C) \rightarrow (\text{POS})$

Given:  $y = (A + \bar{B} + C)(A + B + C)(\bar{A} + \bar{B} + C)$

$$\begin{array}{c} \downarrow \quad \downarrow \quad \downarrow \\ M_2 \quad M_0 \quad M_6 \end{array}$$

Corresponding Maxterms

$$y = M_2 \cdot M_0 \cdot M_6$$

$$y = \prod M(0, 2, 6)$$

Product of maxterm.



Semester: \_\_\_\_\_ Subject: LD Academic Year: \_\_\_\_\_

\* Standard SOP expression for given truth table

steps

- 1) From the given truth table, consider only those combinations of inputs which produce an OIP  $y=1$
- 2) Write the product terms for each combination
- 3) The product terms should be ORed to get the canonical SOP form.

ex 1]

A	B	y
0	0	0
0	1	1
1	0	1
1	1	0

I<sup>st</sup> step - consider those combinations who produce OIP 1

II<sup>nd</sup> step -  $y_1 = \bar{A}B$  ] Boolean expressions  
 $y_2 = A\bar{B}$  ] in the product forms

III<sup>rd</sup> step

$$y = y_1 + y_2 = \bar{A}B + A\bar{B}$$

$$y = m_1 + m_2 \Leftrightarrow$$

$$y = \sum m(1, 2)$$



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

II] To write a standard pos expression for given truthtable

Steps

- 1] From the given truthtable, consider only those o/p which produce 0 (low)
- 2) Write the only maxterms for such combinations
- 3) AND these maxterms to obtain the expression in standard pos Form

ex] Given truthtable

A	B	C	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Annotations:

- Row 1:  $A + B + C \text{ (M}_0\text{)}$
- Row 4:  $A + \bar{B} + \bar{C} \text{ (M}_3\text{)}$
- Row 6:  $\bar{A} + B + \bar{C} \text{ (M}_5\text{)}$
- Row 7:  $\bar{A} + \bar{B} + C \text{ (M}_6\text{)}$

$$y = (A + B + C) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + B + \bar{C}) \cdot (\bar{A} + \bar{B} + C)$$
$$\downarrow \quad \downarrow \quad \downarrow \quad \downarrow$$
$$M_0 \quad M_3 \quad M_5 \quad M_6$$

$$y = M_0 \cdot M_3 \cdot M_5 \cdot M_6$$

$$y = \prod M (0, 3, 5, 6)$$



Semester: III

Subject: LD

Academic Year: 17-18

## \* Karnaugh Map [K-Map]

- It contains boxes or cells
- Number of boxes is equal to  $2^n$

$$1 \text{ iIP variable } 2^1 = 2$$

A	$\bar{A}$	A
0	1	

$$2 \text{ iIP variable } 2^2 = 4$$

A	$\bar{B}$	B
$\bar{A}$	$\bar{A}\bar{B}$	$\bar{A}B$
A	$A\bar{B}$	AB

$$3 \text{ iIP variables } 2^3 = 8$$

AB	00	01	11	10
0				
1				

$$4 \text{ iIP variables } 2^4 = 16$$

AB:	00	01	11	10
CD:	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

- It is important that when we move from one cell to next cell along row or column only one variable in the product term changes.





Semester: \_\_\_\_\_

Subject: \_\_\_\_\_


Academic Year: \_\_\_\_\_

\* Relation bet'n a truth-table & k-map

I] 2 - Variables

Truth Table


A	B	y
0	0	0
0	1	0
1	0	0
1	1	1

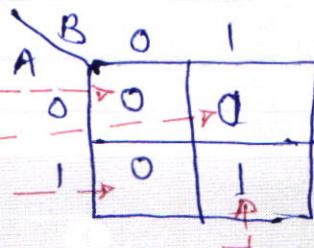

Inside the cells we have to enter the values of OIP corresponding to different combinations of IIP's

II] 3 - Variables

A	B	C	y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

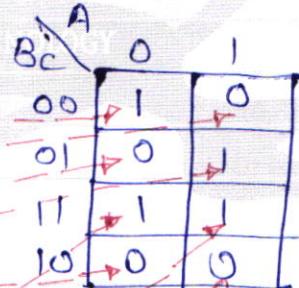

Inside the boxes we have to enter the values of OIP corresponding to different combinations of A & B & C





Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

III 4 - variables k-map

A	B	C	D	y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

Diagram illustrating a 4-variable Karnaugh map (K-map) for the function  $y$ . The K-map has four columns labeled  $A$ ,  $B$ ,  $C$ , and  $D$ , and four rows labeled  $0000$ ,  $0001$ ,  $0011$ , and  $0010$ . The output  $y$  is 1 for the cells  $0000$ ,  $0011$ ,  $0010$ ,  $0111$ ,  $0110$ ,  $1111$ ,  $1110$ , and  $1101$ . The K-map is overlaid with a grid of red boxes, each containing a '1'. The columns are labeled  $CD$  and the rows are labeled  $AB$ .

Inside the boxes we have to enter the values of Q1P corresponding of to different combinations of A,B,C & D





Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

\* Representation of standard SOP form on K-map

- In the K-map by simply entering 1's in the cells of the K-map corresponding to each minterm present in the eqn.
- Remaining boxes are filled with zero (0).

ex)  $y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + AB\bar{C} + ABC$

- Given expression in the std. SOP.
- Each term represents in minterm.
- We have to enter 1's in the cells corresponding to each minterm.

$$2^3 = 8$$

IIP variables are A, B & C

		BC	$\bar{B}\bar{C}$	$\bar{B}C$	BC	$B\bar{C}$
		00	01	11	10	
A	0	1	0	1	1	3
	1	1	4	5	1	7
					1	6

Labels below the K-map:

- $\bar{A}\bar{B}\bar{C}$  (top-left cell)
- $\bar{A}\bar{B}C$  (cell 0)
- $\bar{A}B\bar{C}$  (cell 1)
- $ABC$  (cell 2)
- $A\bar{B}\bar{C}$  (cell 3)



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

\* Simplification of Boolean expression using K-map

Rules

- It is based on combining or grouping the terms in the adjacent cells (or boxes) of k-map.
- 2 cells of k-map are said to be adjacent if they differ in only one variable.
- Horizontal & vertical cells are adjacent cells on left & right or Top & bottom of cells are adjacent cells.
- but the cells connected diagonally are not adjacent ones.
- Group should be as large as possible
- Every must be in at least one group
- Overlapping allowed
- Wrap around allowed.

1) Pair (2) → It is a group of two adjacent 1's in a k-map

- It eliminate one variable in SOP form

2) Quad (4) → Group of Four adjacent 1's on k-map is known as quad

- It is eliminate two variable

3) Octet :— Group of eight adjacent 1's on k-map is known as octet.

- It eliminate three variables.



Semester: \_\_\_\_\_

Subject: LD

Academic Year: \_\_\_\_\_

## \* Minimization of SOP Expression


ex 1] A logical expression in std form

$$y = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C}$$

minimize it using k-map simplification

→  $y = \underbrace{\bar{A}\bar{B}\bar{C}}_{m_0} + \underbrace{\bar{A}B\bar{C}}_{m_2} + \underbrace{\bar{A}BC}_{m_3} + \underbrace{A\bar{B}\bar{C}}_{m_5}$


$$y = \Sigma m(0, 2, 3, 5)$$

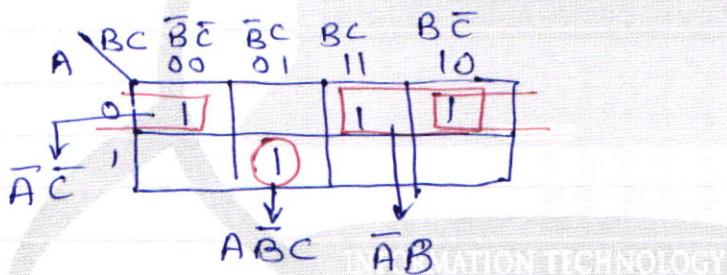

minimized expression in

$y = \bar{A}B + \bar{A}\bar{C} + A\bar{B}\bar{C}$

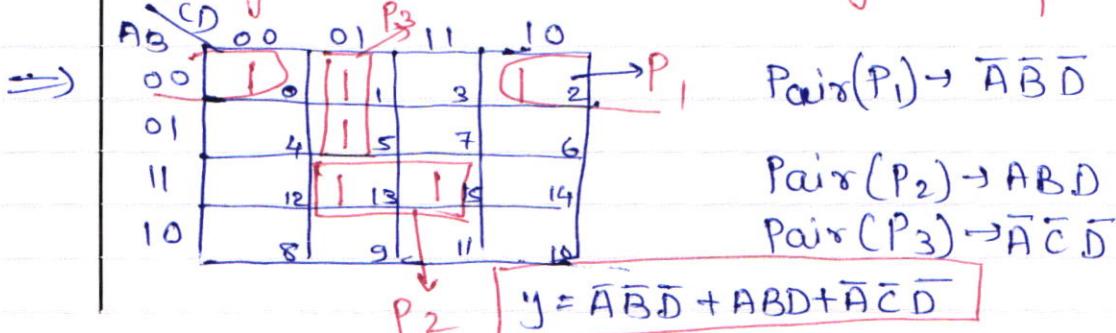ex 2]  $y = \Sigma m(0, 1, 2, 5, 13, 15)$  draw the k-map & find the minimized logical expression






Semester: \_\_\_\_\_

Subject: LD

Academic Year: \_\_\_\_\_

Ex 3]  $y = \Sigma m(1, 3, 4, 5, 7, 9, 11, 13, 15)$   
 Realize this expression using minimum number of gates.
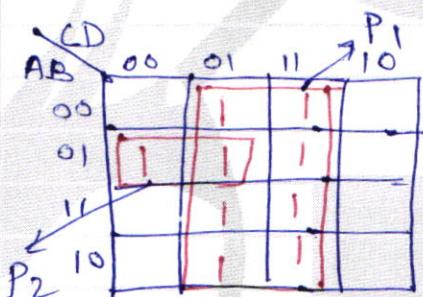
$$\rightarrow y = \Sigma m(1, 3, 4, 5, 7, 9, 11, 13, 15)$$




$$P_1 (\text{Octet}) = D$$

$$P_2 (\text{Pair}) = \overline{ABC}$$


$$y = \overline{ABC} + D$$

Realization with minimum gates

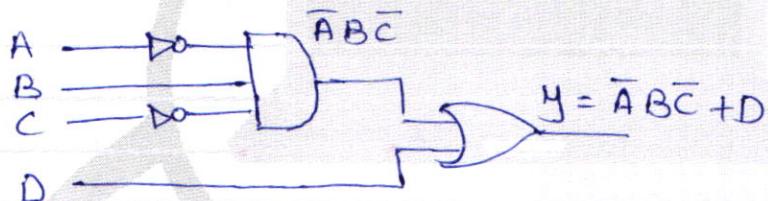

Ex 4]  $y = \Sigma m(1, 2, 9, 10, 11, 14, 15)$   
 Using minimum number of gates

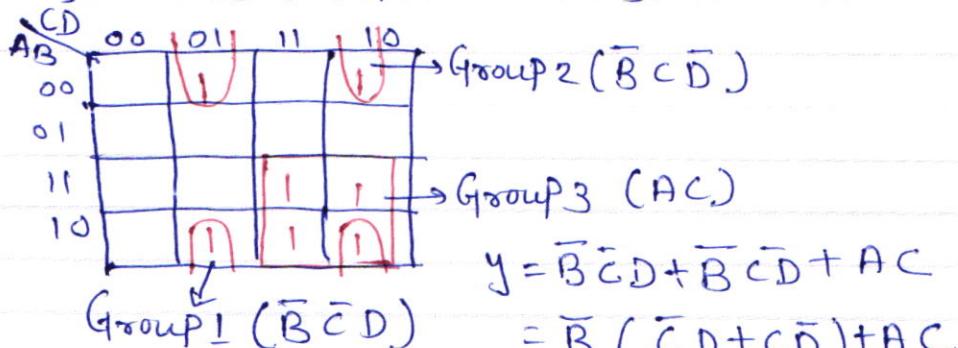
$$\Rightarrow y = \Sigma m(1, 2, 9, 10, 11, 14, 15)$$




$$\begin{aligned}
 y &= \overline{B}\overline{C}D + \overline{B}C\overline{D} + AC \\
 &= \overline{B}(\overline{C}D + C\overline{D}) + AC
 \end{aligned}$$

EX-OR gate

$$y = \overline{B}(C \oplus D) + AC$$

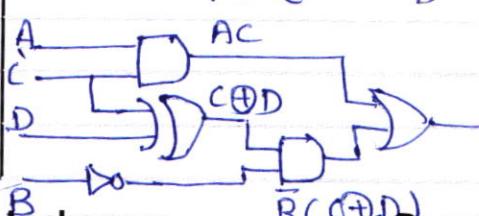

 



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

\*

### Don't Care Condition :-

- In such condition the designer has flexible to assume 0 or 1 as 0/1 for these combination. This condition is known as don't care condn.
- It is represented by (X) cross mark in the cell.
- (X) mark in cell may be assumed to be 1 or 0 depending upon which one leads to a simpler expression.

ex:-

In the terms of minterms f don't Care condn.

$$F(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + d(0, 2, 5)$$

⇒  $\begin{array}{c|ccccc} & & CD \\ & & \diagdown & \diagup & & \\ AB & \diagup & 00 & 01 & 11 & 10 \\ \hline 00 & |X| & 1 & |1| & |X| & - \\ 01 & |X| & - & |1| & - & - \\ 11 & - & |1| & - & - & - \\ 10 & - & |1| & - & - & - \end{array}$

$P_1 \rightarrow \bar{A}\bar{B}$

$y = \bar{A}\bar{B} + cD$

$P_2 \rightarrow ED$

Note :- Every don't care marks need not be considered while grouping.




Semester: \_\_\_\_\_

Subject: \_\_\_\_\_


Academic Year: \_\_\_\_\_

Ex 2] Using K-map simplify
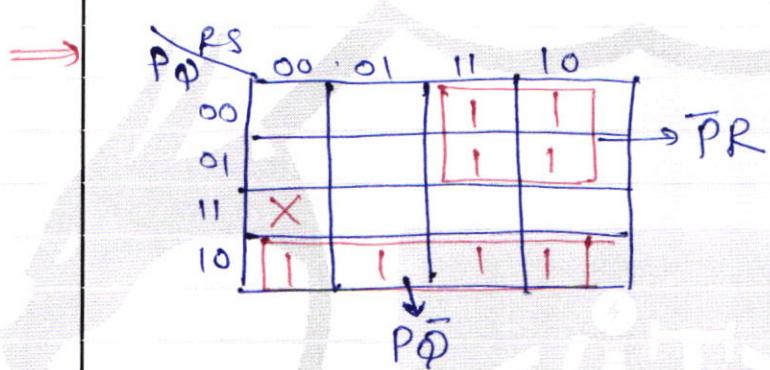
$$F(P, \bar{P}, R, S) = \Sigma m(2, 3, 6, 7, 8, 9, 10, 11) + d(12)$$



$$y = P\bar{Q} + \bar{P}R$$

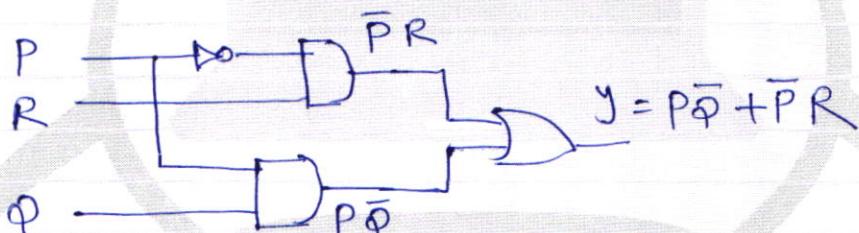

Realization of gates.



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_


Academic Year: \_\_\_\_\_

\* NAND - NAND Implementation  
steps

- 1) Simplify the given logical expression & convert it in the SOP form
- 2] Draw the AND-OR-NOT realization
- 3) Replace every AND gate by a NAND, every OR " " bubbled OR " NOT " " NAND Inverter
- 4) Draw the ckt using only NAND gates.

ex] Implement the following expression using NAND-NAND logic.

$$y = \Sigma m(0, 1, 5)$$

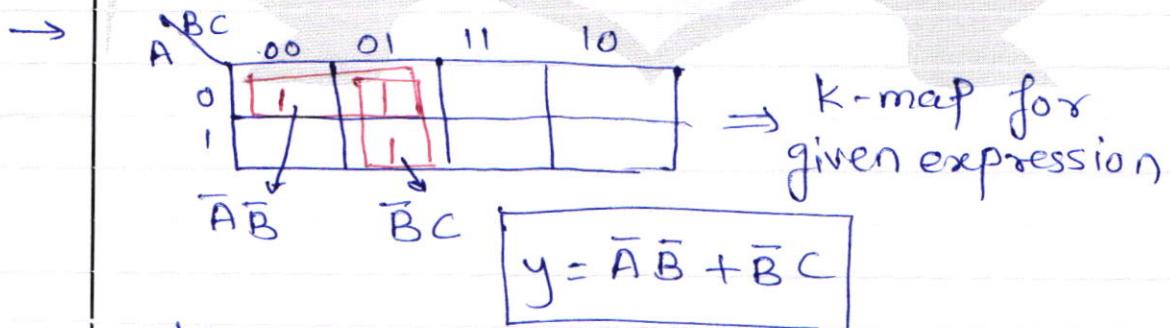


2<sup>nd</sup> step → Implement Using AND-OR-NOT logic gates.




Semester: \_\_\_\_\_

Subject: \_\_\_\_\_


Academic Year: \_\_\_\_\_

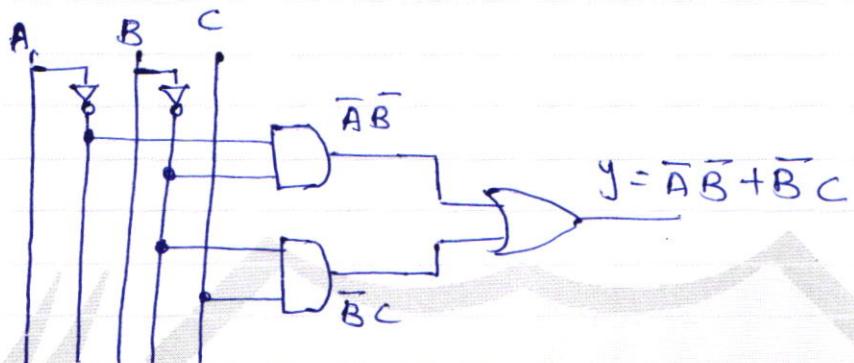


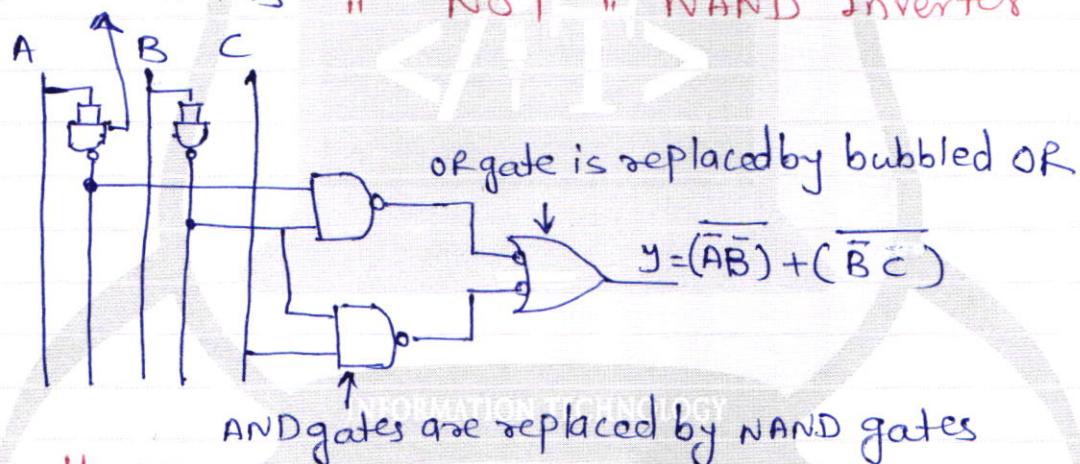3rd step Replace AND by NAND  
 NAND Inverters      " OR by bubbled OR  
                       " NOT " NAND Inverter



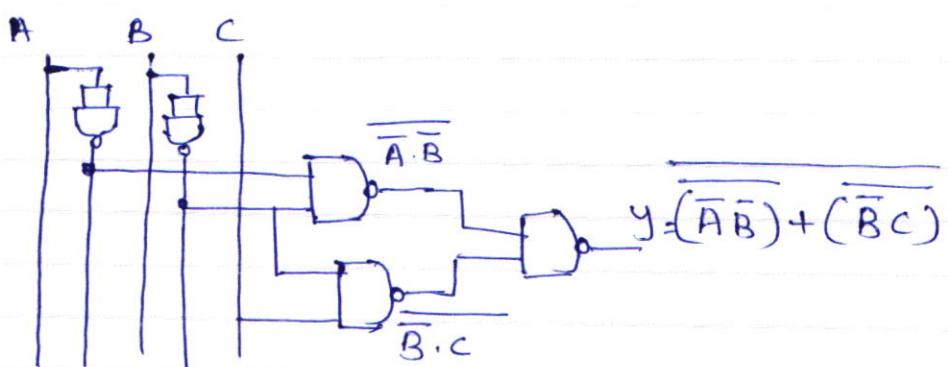4th Step Draw the ckt Using only NAND gates



 



Semester: III

Subject: LD

Academic Year: 17-18

\* NAND-NAND Implementation

Steps:

- 1) Simplify the given logic expression & convert in the SOP Form
- 2) Draw the AND-OR-NOT realization
- 3) Replace 1) every AND gate by NAND  
2) " OR " .. bubbled OR  
3) " NOT " " NAND Inverter
- 4) Draw the ckt using only NAND gates.

ex)  $F(A, B, C, D) = \cdot (0, 1, 2, 3, 4, 7, 8, 11, 12, 15)$   
using NAND-NAND Implementation

→ I<sup>st</sup> step → k-map

AB		CD					
0	1	0	1	0	1	0	1
0	1	0	1	0	1	0	1
1	0	1	0	1	0	1	0
0	1	1	0	0	1	1	0
1	0	0	1	1	0	0	1
0	1	1	0	1	0	0	1
1	0	0	1	0	1	1	0

$A+B$  →  $\overline{A} + \overline{B}$

$C+D$  →  $\overline{C} + \overline{D}$

$$F(A, B, C, D) = (C+D)(\overline{C}+\overline{D})(A+B)$$



Semester: \_\_\_\_\_


Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

II<sup>nd</sup> step


Make the ckt using  
AND - OR - NOT
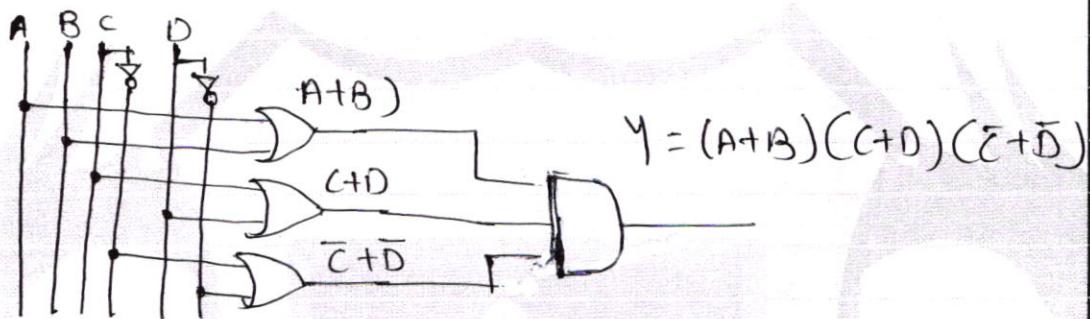
$$F(A, B, C, D) = (A+B)(C+D)(\bar{C}+\bar{D})$$




III<sup>rd</sup> step

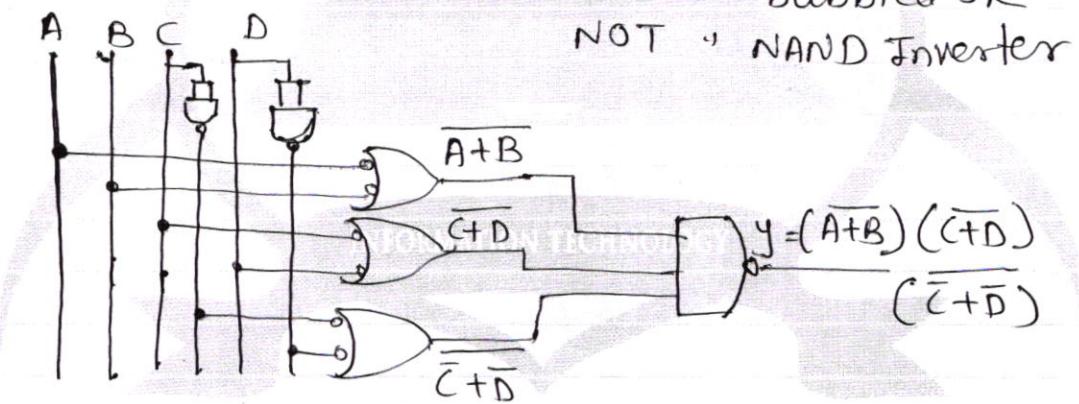Replace  
AND by NAND  
OR " bubbled OR  
NOT " NAND Inverter



IV<sup>th</sup> step

circuit using only NAND gates

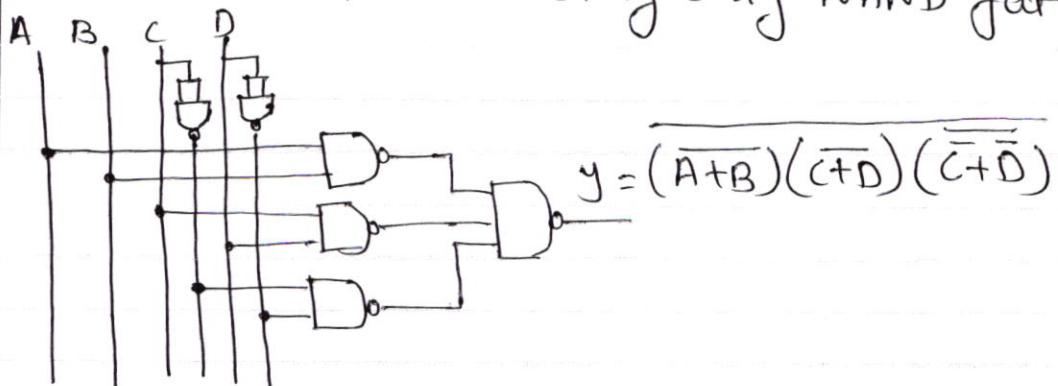





Semester: \_\_\_\_\_

Subject: LD

Academic Year: \_\_\_\_\_

\* NOR-NOR Implementation:


Steps

- 1] Simplify the given logical expression & convert it into product of sum (POS) form
- 2] Draw the ckt using AND-OR-NOT gates
- 3] Replace every OR gate by NOR  
    " AND "     " bubbled AND  
    " NOT "     " NOR inverter  
Then replace every bubbled AND gate by a NOR gate.
- 4] Draw the final ckt using only the NOR gates.

Ex] Implement the following POS expression using NOR-NOR logic

$$F = \prod M(0, 1, 2, 4, 6)$$

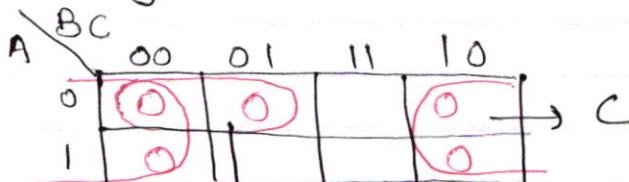→ Step I: Simplify the given fu<sup>n</sup> using k-map



$A+B$

$$F = (A+B) C$$




Semester: \_\_\_\_\_


Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

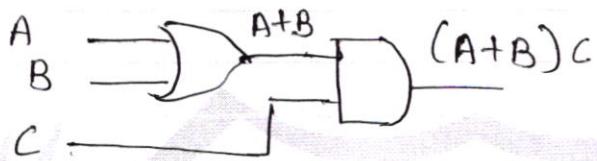
Step II Draw ckt by using AND-OR-NOT gates.



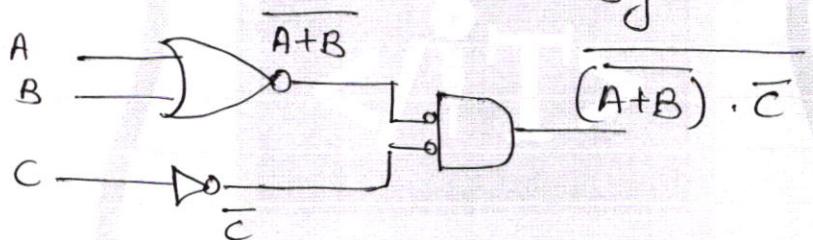Step III Replace OR by NOR  
AND by bubbled AND  
NOT by NOR Inverter



Step IV use only NOR gates

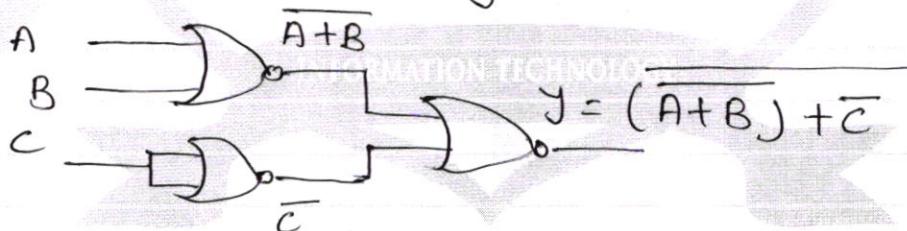



Semester: III

Subject: LD

Academic Year: 17-18



### Quine Mc-cluskey

- 1] It is minimization Technique
- 2] It is Tabular Method
- 3] It should have Capability of large no. of variables
- 4] It should ensure minimized expression
- 5] It should be suitable For Computer sol'n

### Definitions

#### Prime Implicant [PI]

It is a group of minterms which can not be combined with any other minterms or groups.

#### Essential Prime Implicant [EPI]

It is prime implicant. It contains at least one minterm which is not contained in any other prime implicant.

- It is based on the concept of Prime Implicants.



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

\* Steps

- 1] Arrange the given minterms in an ascending order & make the groups based on the number of ones present in their binary presentations, so, there will be at most  $n+1$  groups. If these are ' $n$ ' boolean variables in a boolean fun or  $m$  bits in the binary equivalent of minterms
- 2] Compose the minterms present in successive groups. If there is Change in only one bit position, then take the pair of those two minterms & place '-' (underscore) this symbol in the differed bit position & keep the remaining bits as it is
- 3] Repeat step 2 with newly formed terms till we get all prime Implicants. Combine the minterm pairs into groups of Four (Quad). & remove the repeated rows
- 4] Formulate the prime implicant table. It consists of set of rows & columns prime implicants can be placed in



Parahyangan Jain Ecological Institute  
**A. P. SHAH INSTITUTE OF TECHNOLOGY**

(Approved by AICTE New Delhi & Govt. of Maharashtra, Affiliated to University of Mumbai)  
(Religious Jain Minority)

Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

rowwise & minterms can be placed in columnwise. Place '1' in the cells corresponding to the minterms that are covered in each prime implicant.

5] Find the Essential prime Implicants [EPI] by observing each column.

If minterm is covered only by one Prime implicant [PI], then it is essential prime implicants [EPI] will be part of the simplified Boolean fu?



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

ex1] Minimize the Logic Fun using  
P-M method

$$F(A, B, C, D) = \Sigma m(1, 3, 7, 9, 10, 11, 13, 15)$$

→ Step I Group the minterms

according to number of 1's

	Group	Minterm	Binary Representation			
			A	B	C	D
one 1's	1	1	0	0	0	1 ✓
Two 1's	2	3	0	0	1	1 ✓
		9	1	0	0	1 ✓
		10	1	0	1	0 ✓
Three 1's	3	7	0	1	1	1 ✓
		11	1	0	1	1 ✓
		13	1	1	0	1 ✓
four 1's	4	15	1	1	1	1 ✓

Step II: Group the minterms  
to form the pairs.



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

Group	Minterms Pair	Binary repn				[PI] prime Implicant
		A	B	C	D	
1	1-3	0	0	-	1	✓
	1-9	-	0	0	1	✓
	3-7	0	-	1	1	✓
	3-11	-	0	1	1	✓
2	9-11	1	0	-	1	✓
	9-13	1	-	0	1	✓
	10-11	1	0	1	-	$\rightarrow A\bar{B}C$
3	7-15	-	1	1	1	✓
	11-15	1	-	1	1	✓
	13-15	1	1	-	1	✓

Step III Group the minterm to form the Quad

Group	Minterms Quad	Binary Repren				prime Implicant
		A	B	C	D	
1	1-3-9-11	-	0	-	1	{ } $\bar{B}D$
	1-9-3-11	-	0	-	1	{ } $C$
2	3-7-11-15	-	-	1	1	{ } $CD$
	3-11-7-15	-	-	1	1	{ } $C$
3	9-11-13-15	1	-	-	1	{ } $AD$
	9-13-11-15	1	-	-	1	{ } $D$



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

now, remove the repeated rows

Group	Minterms	A	B	C	D	PI
1	1-3-9-11	-	0	-	1	$\bar{B}D$
2	3-7-11-15	-	-	-	1	$CD$
3	9-11-13-15	1	-	-	1	$AD$

Step IV: Prepare the table of prime implicants.

Prime Implicants	Decimal no's.	1	3	7	9	10	11	13	15
$A\bar{B}C$	10-11					1	1		
$\bar{B}D$	1-3-9-11	1	1	1	1				
$CD$	3-7-11-15		1	1			1	1	
$AD$	9-11-13-15				1	1	1	1	

Essential prime Implicants (EPI). They cover minterms 1, 3, 7, 9, 10, 11, 13, 15. encircled numbers are EPI.

$$F(A, B, C, D) = A\bar{B}C + \bar{B}D + CD + AD$$




Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

Now, we can crosscheck by using  
K-map

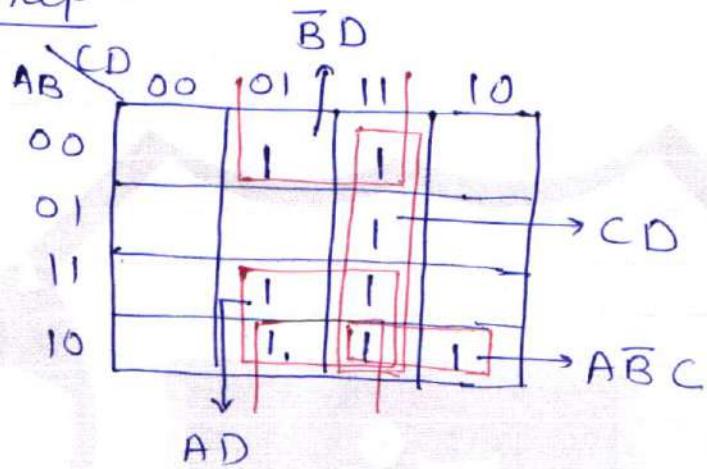

$$F(A, B, C, D) = A\bar{B}C + A\bar{D} + \bar{C}D + \bar{B}D$$

ex<sup>2</sup>]  $F(W, X, Y, Z) = \Sigma m(2, 6, 8, 9, 10, 11, 14, 15)$

using Q-M tabular Method

→ Step I: Arrange all minterms according to no. of 1's contained & form the groups have no ones, one 1's, two 1's & so on

Group	Minterms	Binary Repres'n			
		W	X	Y	Z
1	2	0	0	1	0
	8	1	0	0	0
2	6	0	1	1	0
	9	1	0	0	1
3	10	1	0	1	0
	11	1	0	1	1
4	14	1	1	1	0
	15	1	1	1	1



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

Step II combine the minterms into a group of two

Group	Minterm matched Pairs	Binary Repres <sup>n</sup>	w	x	y	z
1	2-6	0	-	1	0	✓
	2-10	-	0	1	0	✓
	8-9	1	0	0	-	✓
	8-10	1	0	-	0	✓
2	6-14	-	1	1	0	✓
	9-11	1	0	-	1	✓
	10-11	1	0	1	-	✓
	10-14	1	-	1	0	✓
3	11-15	1	-	1	1	✓
	14-15	1	1	1	-	✓

Step III: combination the min term pairs into groups of four (Quad.)

Group	Minterm (Group of four)	Binary repres <sup>n</sup>	w	x	y	z	P I
1	2-6-10-14	- - 1 0	-	-	1	0	$\rightarrow Y\bar{Z}$
	2-10-6-14	- - 1 0	-	-	1	0	
	8-9-10-11	1 0 - -	1	0	-	-	$\rightarrow W\bar{X}$
	8-10-9-11	1 0 - -	1	0	-	-	
2	10-11-14-15	1 - 1 -	1	-	1	-	
	10-14-11-15	1 - 1 -	1	-	1	-	$\rightarrow WY$



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

now, remove the repeated rows

Group	minterms	w	x	y	z	PI
1	2-6-10-14	-	-	1	0	$y\bar{z}$
	8-9-10-11	1	0	-	-	$w\bar{x}$
2	10-11-14-15	1	-	1	-	$wy$

Prime Implicants are  $\rightarrow y\bar{z}, w\bar{x}, wy$

Step IV: - The Prime Implicant table is shown below

Prime Implicant	Decimal no's	Given minterms
$y\bar{z}$	2-6-10-14	1 1 1 1
$w\bar{x}$	8-9-10-11	1 1 1 1
$wy$	10-11-14-15	1 1 1 1

In this example, we got three PI & all the three are essential.

∴ the simplified boolean f'n is

$$F(w, x, y, z) = y\bar{z} + w\bar{x} + wy$$



Semester: III

Subject: LD

Academic Year: \_\_\_\_\_

Cross check by using K-map

$F(w, x, y, z) = (2, 6, 8, 9, 10, 11, 14, 15)$   
 in SOP form

$wx\bar{y}\bar{z}$	$\bar{w}\bar{x}\bar{y}\bar{z}$	$\bar{w}x\bar{y}\bar{z}$	$w\bar{x}\bar{y}\bar{z}$	$wx\bar{y}\bar{z}$
00	01	11	10	11
0	1	3	1	2
4	5	7	1	6
12	13	15	1	14
1	1	1	1	1
8	9	11	10	10

$$F(w, x, y, z) = w\bar{x} + \bar{y}\bar{z} + w\bar{y}$$

ex3] Minimal expression using  $\Phi$ -M method

$$F(A, B, C, D) = \Sigma m(1, 5, 6, 12, 13, 14) + d(2, 4)$$

→ Step I: Group the minterms according to no. of 1's

Group	Minterm	Binary Representation			
		A	B	C	D
1	1	0	0	0	1
	2 * don't care	0	0	1	0
	4 * care	0	1	0	0
2	5	0	1	0	1
	6	0	1	1	0
	12	1	1	0	0
3	13	1	1	0	1
	14	1	1	1	0



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_

Step II: Group the minterms to form

Pairs

Group	Minterms Pairs	Binary Repre <sup>n</sup>				Prime Implicant
		A	B	C	D	
1	1-5	0	-	0	1	$\bar{A}\bar{C}D$
	2-6	0	-	1	0	$\bar{A}C\bar{D}$
	4-5	0	1	0	1	✓
	4-6	0	1	-	0	✓
	4-12	-	1	0	0	✓
2	5-13	-	1	0	1	✓
	6-14	-	1	1	0	✓
	12-13	1	1	0	-	✓
	12-14	1	1	-	0	✓

Step III: Group the minterms to form Quad (Four)

Group	Minterm Four	Binary repre <sup>n</sup>				Prime Implicant
		A	B	C	D	
1	4-5-12-13	-	1	0	-	$B\bar{C}$
	4-6-12-14	-	1	-	0	$B\bar{D}$
	4-12-5-13	-	1	0	-	$\bar{B}\bar{C}$
	4-12-6-14	1		0		$B\bar{D}$

Step IV: Prime Implicants

$$F(A, B, C, D) = \bar{A}\bar{C}D + \bar{A}C\bar{D} + B\bar{C} + B\bar{D} \\ + B\bar{C} + B\bar{D}$$

$$\therefore \bar{B}\bar{C} + B\bar{C} = B\bar{C} \\ \bar{B}\bar{D} + B\bar{D} = B\bar{D}$$

$$F(A, B, C, D) = \bar{A}CD + \bar{A}C\bar{D} + B\bar{C} + B\bar{D}$$



Semester: \_\_\_\_\_

Subject: \_\_\_\_\_

Academic Year: \_\_\_\_\_


Step II: Prepare the table for Prime Implicants

Prime Implicant	minterms	Given Minterms				
$\bar{A} \bar{C} D$	1-5	1	1			
$\bar{A} C \bar{D}$	2*-6			1		
$B \bar{C}$	4*-5-12-13		1	1	1	
$B \bar{D}$	4*-6-12-14			1	1	1

$$f(A, B, C, D) = \bar{A} \bar{C} D + B \bar{C} + B \bar{D} \rightarrow EPI$$

- Don't Care terms are not listed in this table.
- Encircled the 1's represents the essential prime Implicants [EPI]

Cross check by using k-map

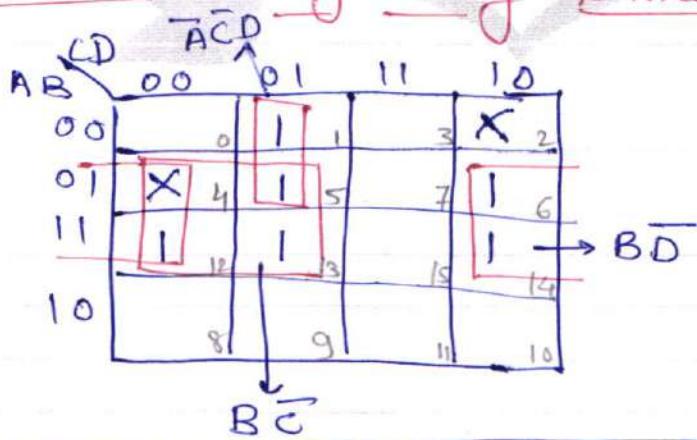

$$f(A, B, C, D) = \bar{A} \bar{C} D + B \bar{C} + B \bar{D}$$